
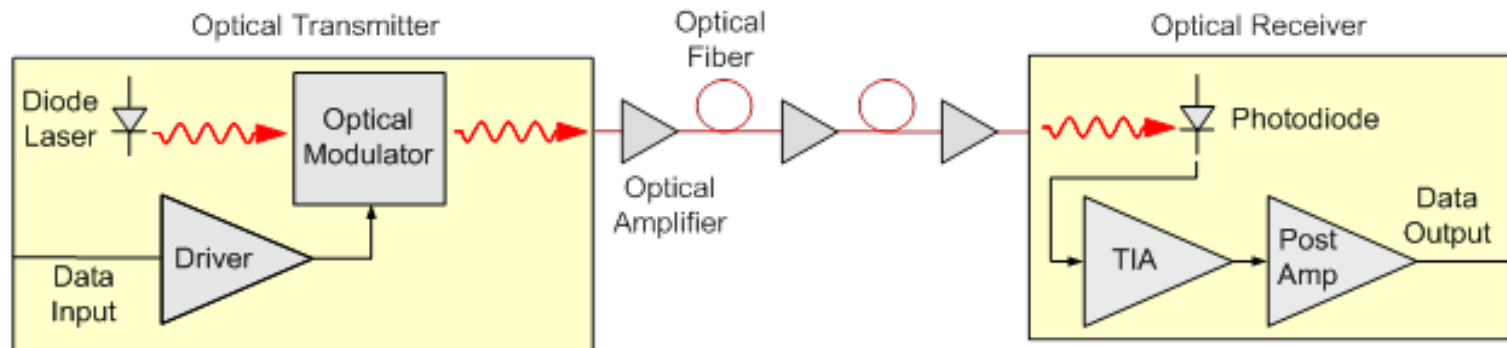


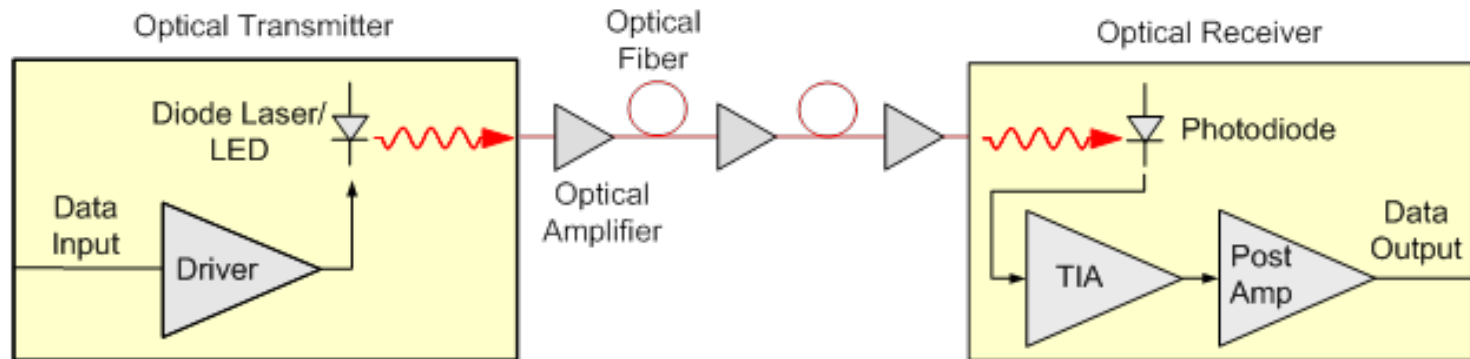Two Main Approaches to Optical Transmission



Why go to the trouble of using an external modulator?


Table 7.1 Maximum (unrepeated) transmission distances over an SMF at $1.55 \mu\text{m}$ for various transmitter types based on Eqs. (7.19), (7.18), and (7.16) with $D = 17 \text{ ps}/(\text{nm} \cdot \text{km})$.

Transmitter Type	2.5 Gb/s	10 Gb/s
Fabry-Perot laser ($\Delta\lambda = 3 \text{ nm}$)	4 km	1 km
Distributed feedback laser ($\alpha = 4$)	230 km	15 km
External modulator ($\alpha = 0$)	960 km	60 km

From Broadband circuits for optical fiber communication, Eduard Säckinger, Wiley 2005

- An external modulator offers extended transmission distance

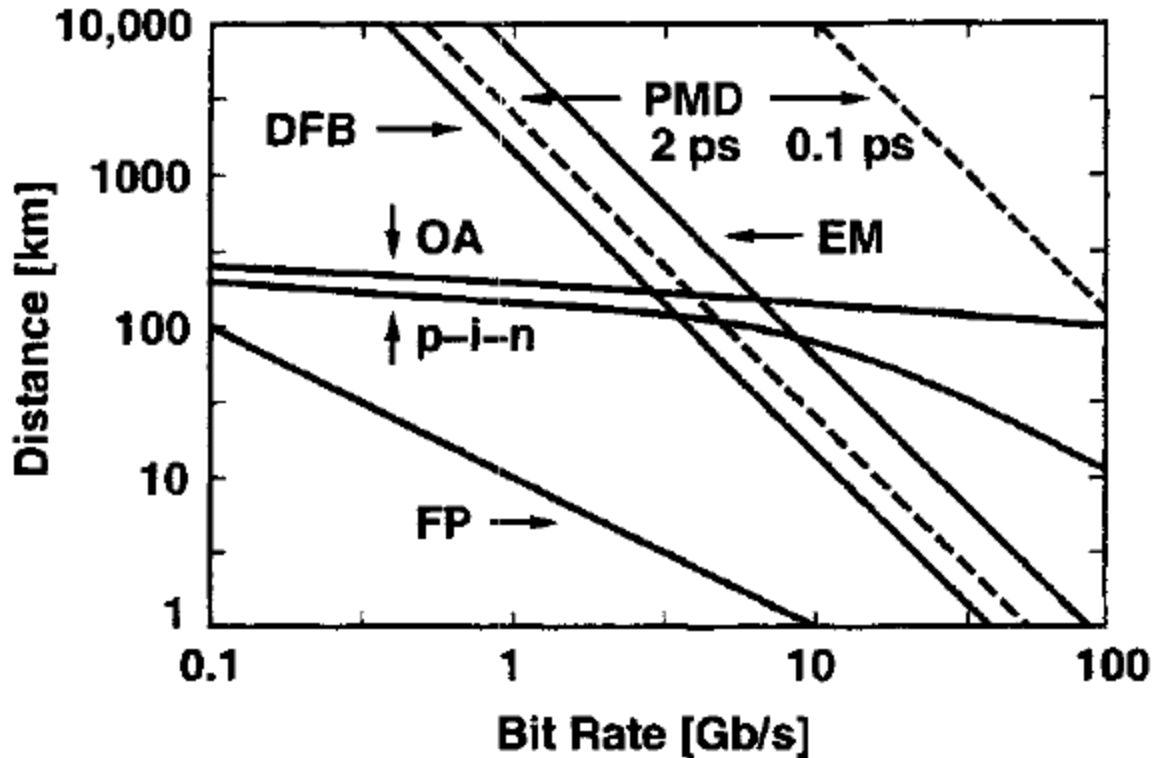More Detailed Limits to Transmission Distance



from Broadband Circuits
for Optical Fiber
Communication, Eduard
Säckinger, Wiley 2005

Limits Due to Chromatic Dispersion

- FP = Fabry Perot Laser
- DFB = Distributed Feedback Laser
- EM = External Modulation


Limits due to Polarization Mode Dispersion

- PMD = Polarization Mode Dispersion

Limits due to Optical Attenuation in Fiber


- p-i-n = Photodetector
- OA = Optically Pre-Amplified Photodetector

The Inside of an Optical Transmitter

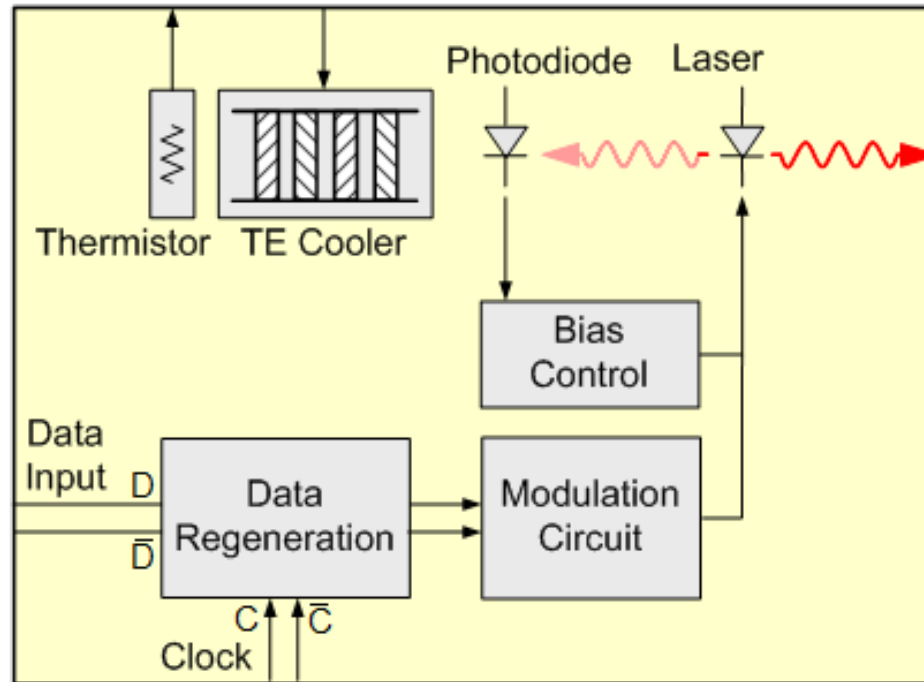


- The transmitter includes components for control of temperature and average power
- A transmitter often contains circuitry for re-shaping and re-timing data

Basic Laser/Modulator Drive Circuitry


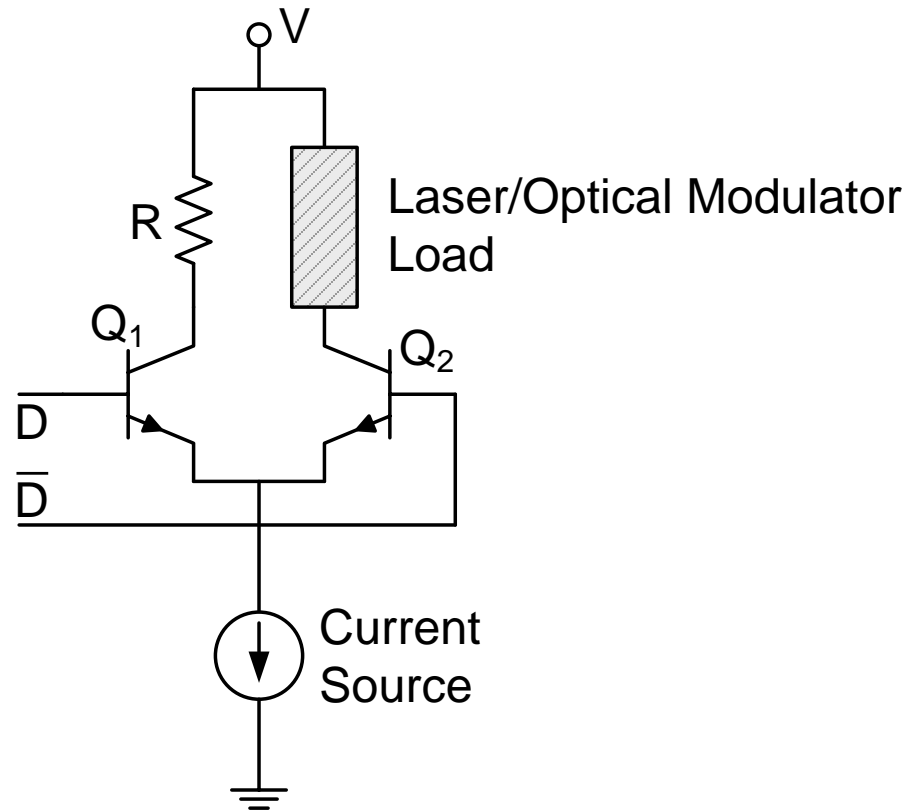


Why do we use current steering?

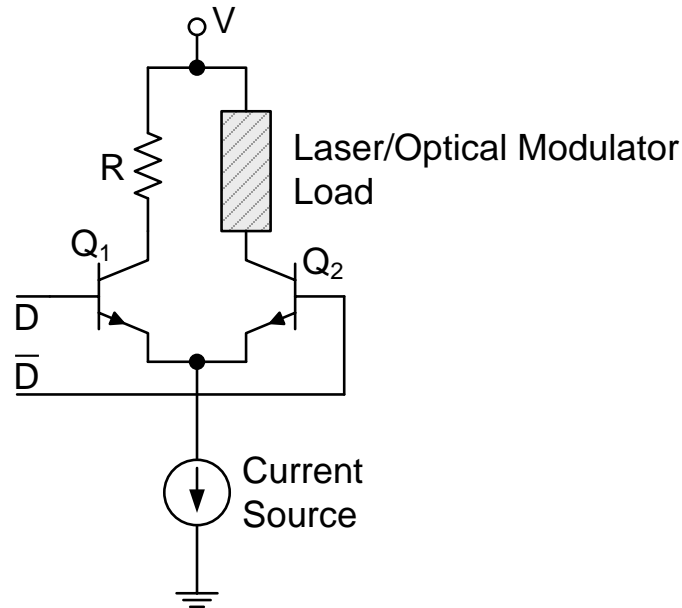

- A constant current to the ground through the current source avoids current transients due to parasitic capacitances and inductances


Why do we use differential input?

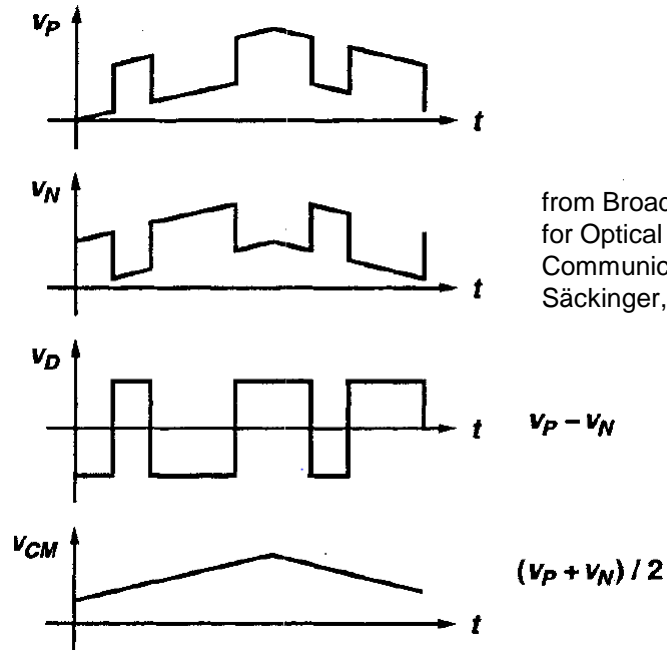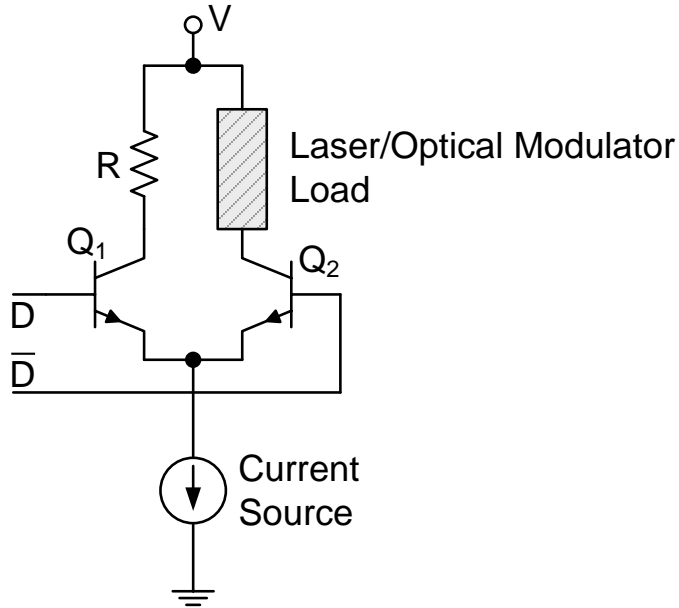

from Broadband Circuits for Optical Fiber Communication, Eduard Säckinger, Wiley 2005


- The differential design is insensitive to common-mode noise and avoids the need for an input reference voltage

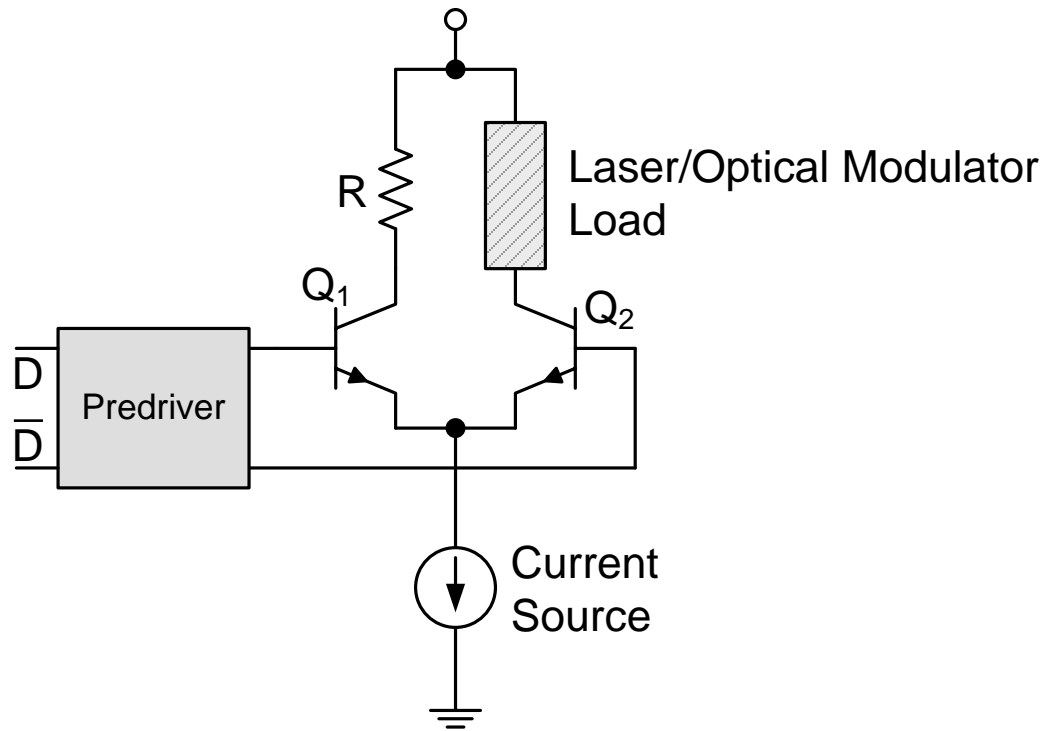Drive Circuitry with an Additional Predriver




- The predriver conditions the signals for input to transistors Q_1 and Q_2

Laser Load for the Drive Circuitry

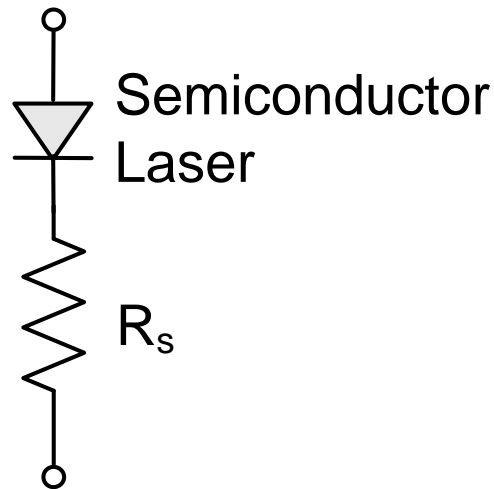

- The resistor R_s , dampens current oscillations due to parasitic inductances in the circuitry

Modulator Load for Drive Circuitry

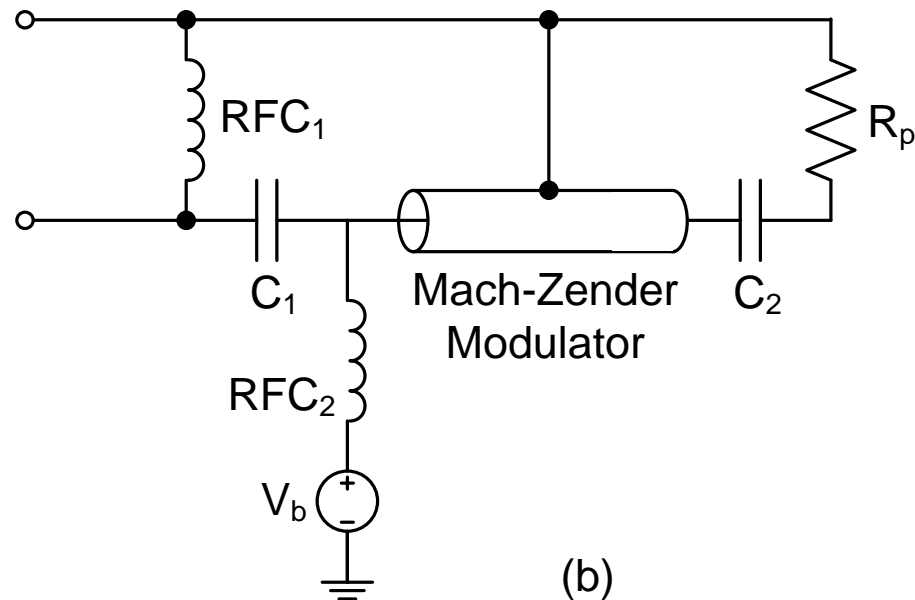

- **Load is a transmission line**
- Modulator is AC coupled to the drive circuitry by inductor RFC_1 (RF Choke 1) and capacitor C_1 (the combination is known as a "Bias T")
- **A Bias voltage V_b** is DC coupled to the modulator by RFC_2
- The drive signal is terminated by the resistor R_p
- The capacitor C_2 blocks DC current through the modulator